
 


Unit-5 : Combinational Circuit

Multiplexers-De-multiplexers
Decoder-Encoder


Multiplexer

 - Also called data selectors.
- **Basic function:** Select one of its 2^n data input lines and place the corresponding information onto a single output line.
- n input bits needed to specify which input line is to be selected.
 - Place binary code for a desired data input line onto its n select input lines.



Typical Application of a MUX

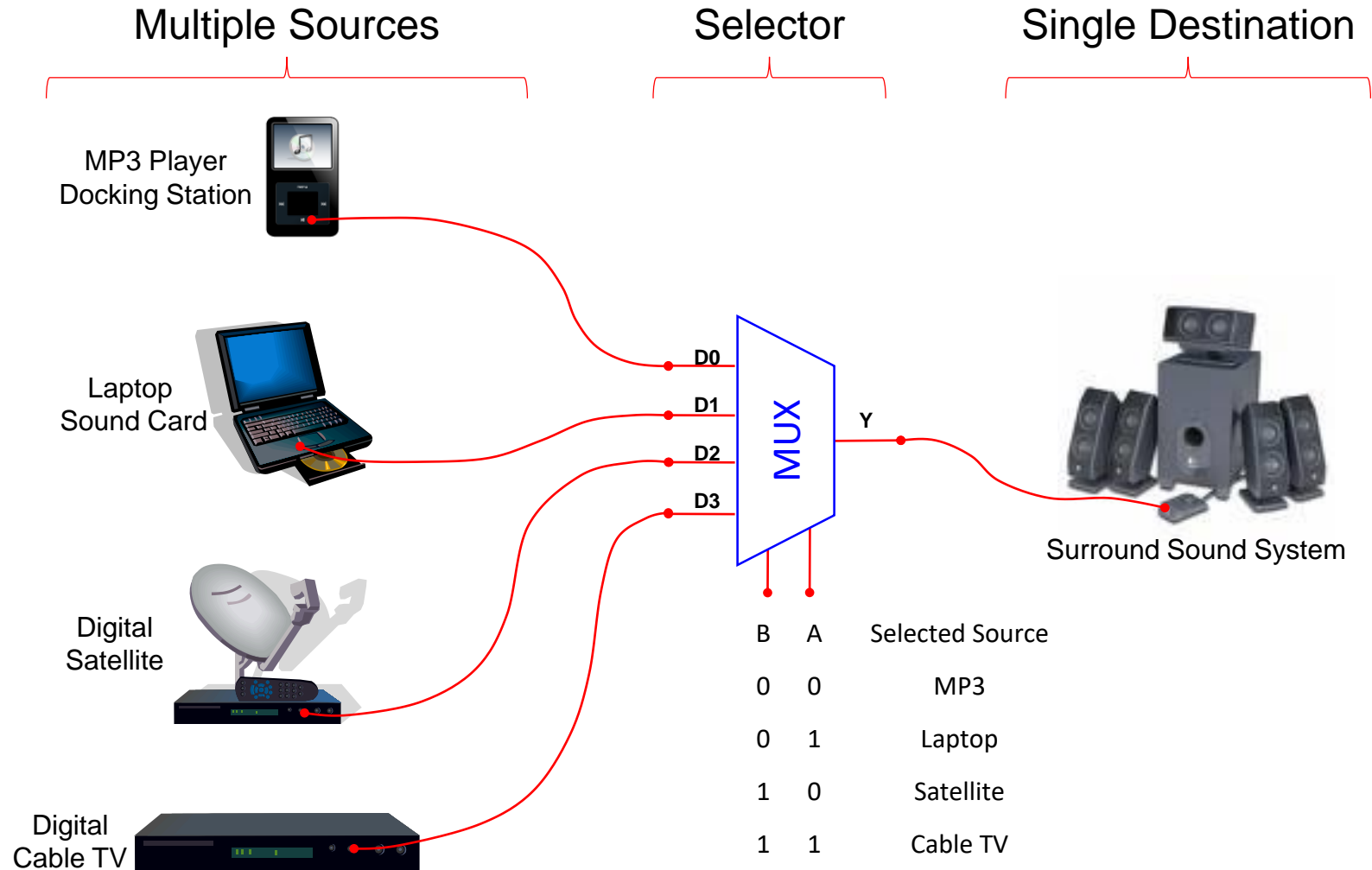- One of the primary applications of multiplexers is to provide for the transmission of information from several sources over a single path. This process is known as **multiplexing**.



MCQ

Q. The two input MUX would have _____


- a) 1 select line
- b) 2 select lines
- c) 4 select lines
- d) 3 select lines

MCQ


Q. 4 to 1 MUX would have _____

- a) 2 inputs
- b) 3 inputs
- c) 4 inputs
- d) 5 inputs

4:1 Multiplexer

 

Selection Lines		Output
S_1	S_0	Y
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

 

$$Y = S_1' S_0' I_0 + S_1' S_0 I_1 + S_1 S_0' I_2 + S_1 S_0 I_3$$

Q. $Y(A, B, C) = \sum m(1, 3, 5, 6)$ implement with 4:1 multiplexer


Q. $Y(A, B, C) = \sum m(1, 2, 4, 5)$ implement with 4:1 multiplexer.

Expression implementation with Multiplexer

Q. $Y(A, B, C) = \sum m(1, 3, 5, 6)$ implement with 4:1 multiplexer

$$Y = \overline{A}\overline{B}C + \overline{A}BC + A\overline{B}C + ABC$$

Any 2 input (AB/BC/AC) select line

 


Rearrange equation with selection line

$$Y = \underbrace{0.(\overline{B}\overline{C})}_{I_0} + \underbrace{\overline{B}C(\overline{A} + A)}_{I_1} + \underbrace{A\overline{B}\overline{C}}_{I_2} + \underbrace{ABC}_{I_3}$$

Q. $Y(A, B, C) = \sum m(1, 2, 4, 5)$ implement with 4:1 multiplexer

$$Y = \overline{A}\overline{B}C + \overline{A}B\overline{C} + A\overline{B}\overline{C} + A\overline{B}C$$

Any 2 input (AB/BC/AC) select line

 


Rearrange equation with selection line

$$Y = \underbrace{\overline{A}\overline{B}C}_{I_0} + \underbrace{\overline{A}B\overline{C}}_{I_1} + \underbrace{A\overline{B}(\overline{C} + C)}_{I_2} + \underbrace{AB.0}_{I_3}$$

MCQ

 The logic function implemented by the circuit below is (ground implies a logic "0")



(A) $F = \text{AND}(P, Q)$


(B) $F = \text{OR}(P, Q)$

(C) $F = \text{XNOR}(P, Q)$

 
(D) $F = \text{XOR}(P, Q)$

Logic Gate implementation with 2:1 Multiplexer

Which logic gate represents by the given multiplexer?



- (a) AND
- (b) OR
- (c) XOR
- (d) NAND

 

- (a) AND
- (b) OR
- (c) XOR
- (d) NAND



Logic Gate implementation with 2:1 Multiplexer

AND GATE

A	B	OUT
0	0	0
0	1	0
1	0	0
1	1	1

OUT = 0
when A = 0

OUT = B
when A = 1

  


NAND GATE

A	B	OUT
0	0	1
0	1	1
1	0	1
1	1	0

OUT = 1
when A = 0

OUT = B'
when A = 1


 


OR GATE

A	B	OUT
0	0	0
0	1	1
1	0	1
1	1	1

OUT = B
when A = 0

OUT = 1
when A = 1

 
 


NOR GATE

A	B	OUT
0	0	1
0	1	0
1	0	0
1	1	0

OUT = B'
when A = 0

OUT = 0
when A = 1

  

Logic Gate implementation with 2:1 Multiplexer

XOR GATE

A	B	OUT
0	0	0
0	1	1
1	0	1
1	1	0

OUT = B when A = 0

OUT = B' when A = 1



XNOR GATE

A	B	OUT
0	0	1
0	1	0
1	0	0
1	1	1


OUT = B' when A = 0

OUT = B when A = 1




NOT GATE

A	OUT
0	1
1	0

 


4:1 Mux using 2:1 Mux

S1 (MSB)	S0(LSB)	Out
0	0	I0
0	1	I1
1	0	I2
1	1	I3

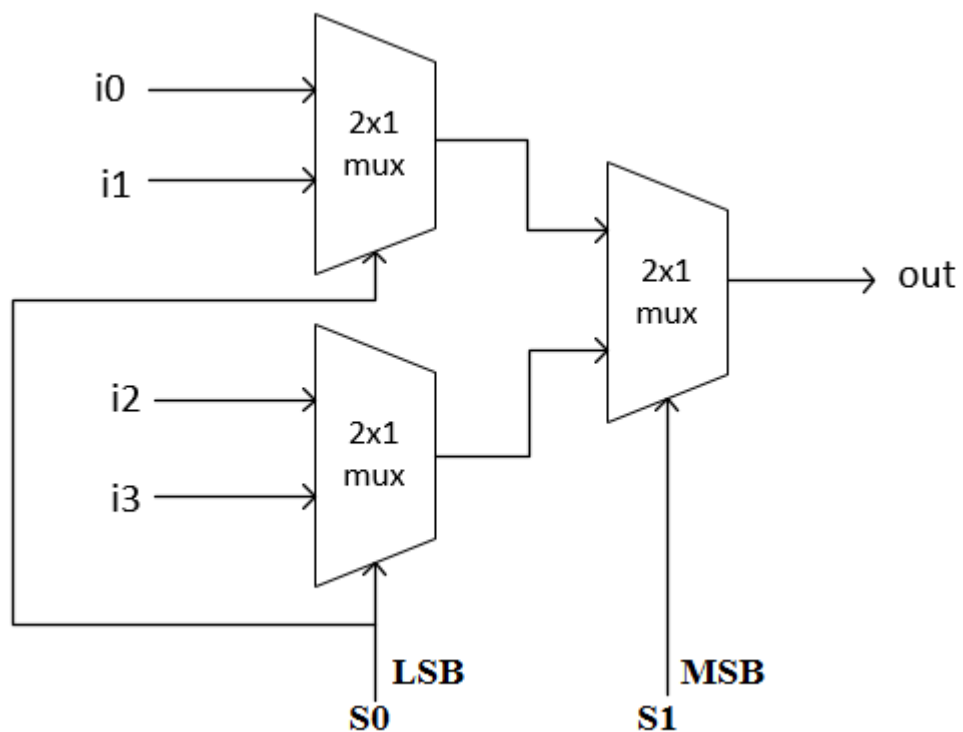

8:1 Mux using 4:1 and 2:1 Mux


Select Data Inputs			Output
S_2	S_1	S_0	Y
0	0	0	D_0
0	0	1	D_1
0	1	0	D_2
0	1	1	D_3
1	0	0	D_4
1	0	1	D_5
1	1	0	D_6
1	1	1	D_7

 


Q. Design 16:1 MUX using 4:1 MUX

 Question:

What will be the expression for the output Z.




8:1 Multiplexer

 


S2	S1	S0	Out
0	0	0	I0
0	0	1	I1
0	1	0	I2
0	1	1	I3
1	0	0	I4
1	0	1	I5
1	1	0	I6
1	1	1	I7
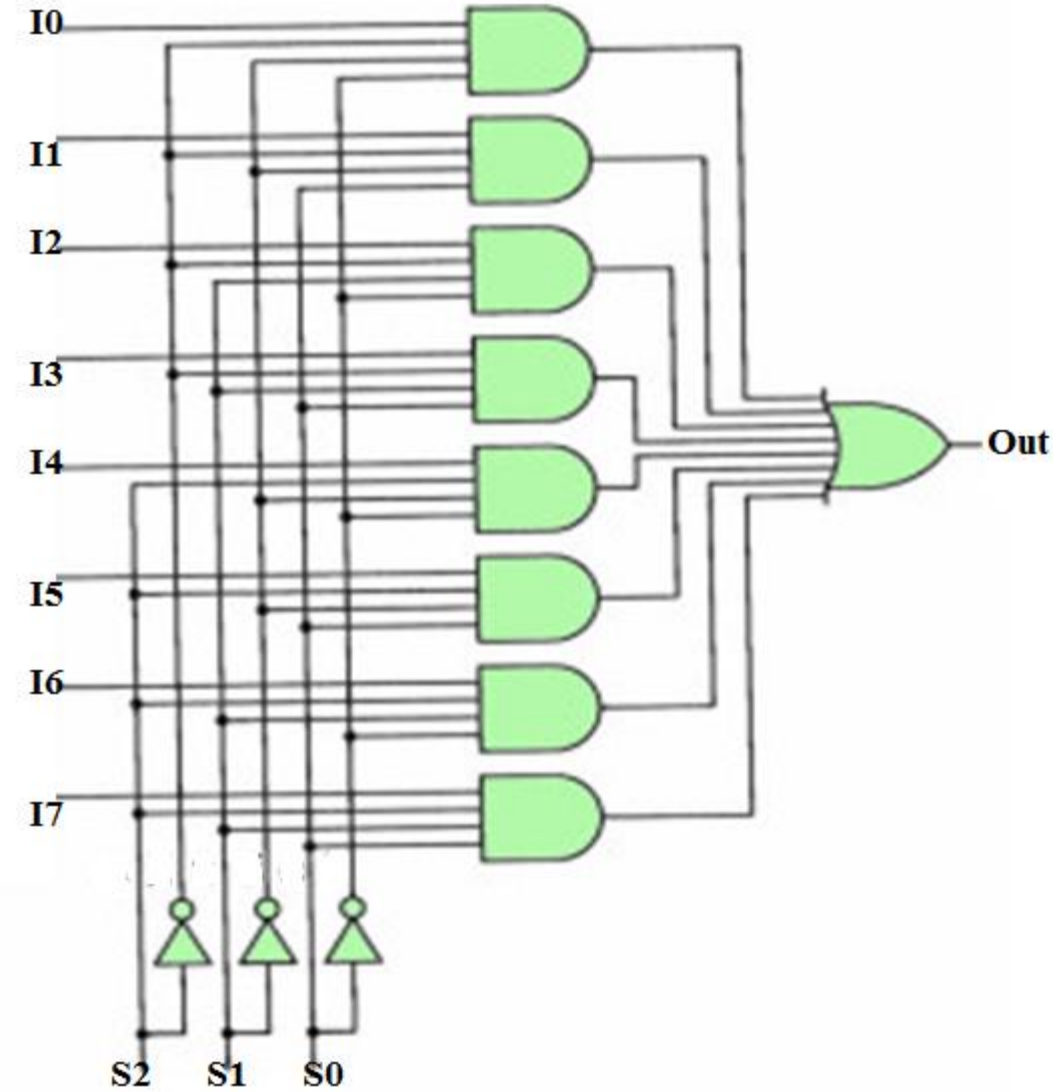
$$\text{Out} = S_2'S_1'S_0'I_0 + S_2'S_1'S_0I_1 + S_2'S_1S_0'I_2 + S_2'S_1S_0I_3 \\ + S_2S_1'S_0'I_4 + S_2S_1'S_0I_5 + S_2S_1S_0'I_6 + S_2S_1S_0I_7$$




De-multiplexer

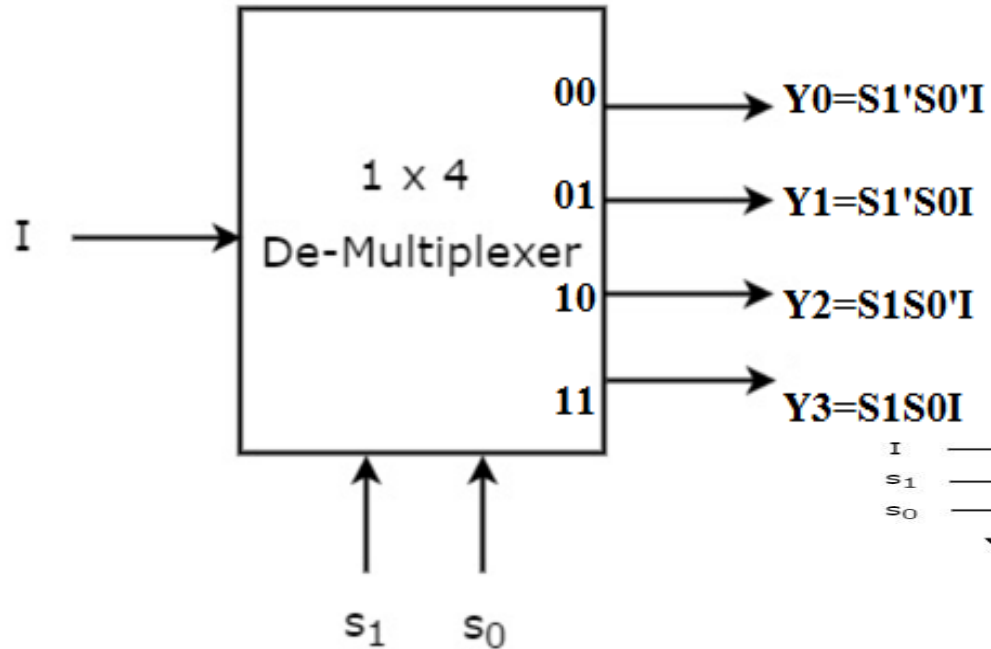
- Switch one common input line to one of several output line based on select input.
- It is data distributor.
- Size of demux $1:2^n$
- Example 1:4, 1:8, 1:16..... Demultiplexer




Selection Inputs		Outputs			
S ₁	S ₀	Y ₃	Y ₂	Y ₁	Y ₀
0	0	0	0	0	I
0	1	0	0	I	0
1	0	0	I	0	0
1	1	I	0	0	0

 

Application

 

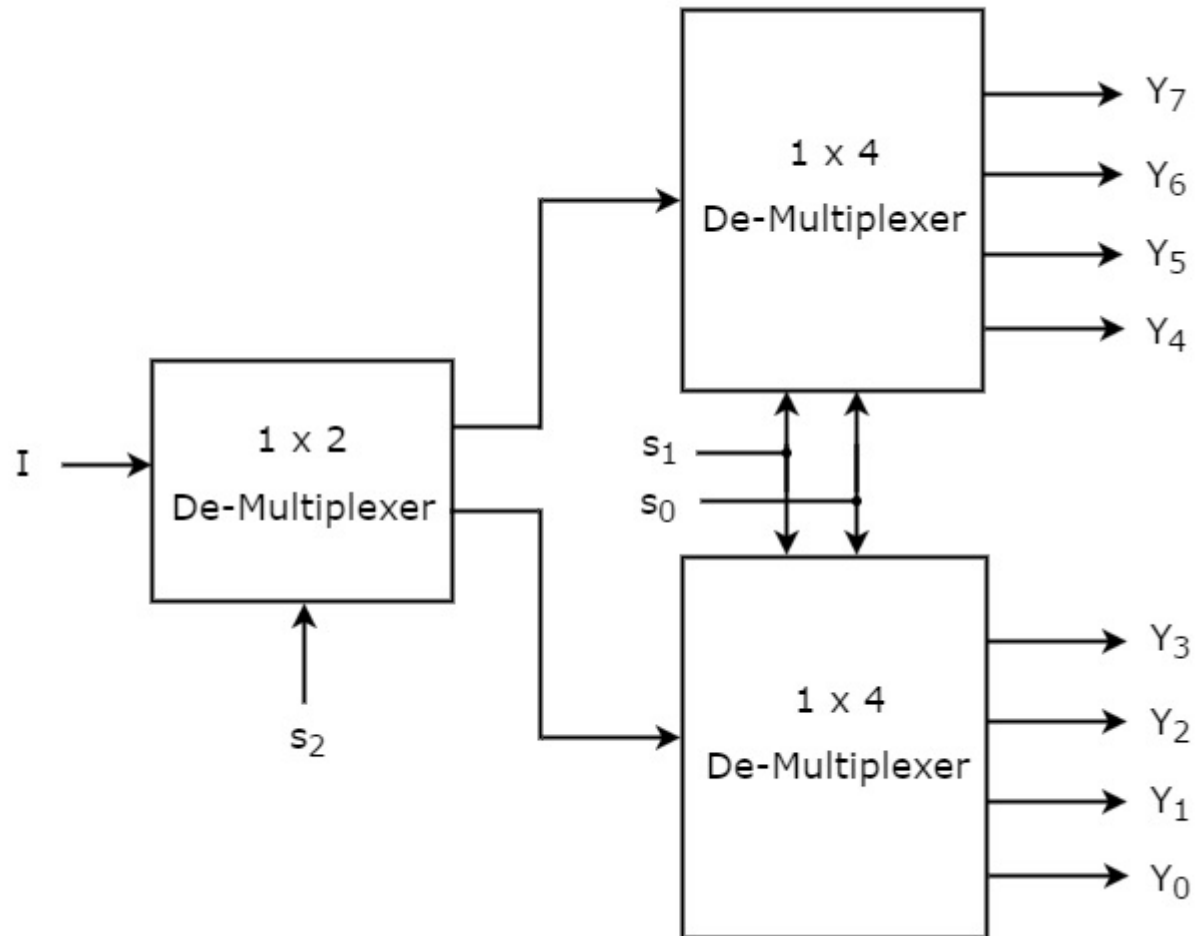1:8 De-Multiplexer using lower order De-Mux




Decoder


- A combinational circuit that has ' n ' input lines and maximum of 2^n output lines.
- One of these outputs will be active High based on the combination of inputs present, when the decoder is enabled.

The outputs of the decoder are **min terms** of ' n ' input variables lines when it is **enabled**.

Size of Decoder are 2:4, 3:8, 4:16....

 

A_1	A_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

 

MCQ

Which one of the following represents the decoder ?

- (a) 4:1
- (b) 1:4
- (c) 3:8
- (d) 8:3


MCQ

How many inputs and outputs for four variable function in a decoder.

 - (a) 4,1
- (b) 4,16
- (c) 3,8
- (d) 16, 1


Full Adder using 3:8 Decoder

$$S = A'B'C + A'BC' + AB'C' + ABC = \Sigma(1,2,4,7)$$
$$CY = A'BC + AB'C + ABC' + ABC = \Sigma(3,5,6,7)$$




Full Subtractor using 3:8 Decoder
 
$$\text{Difference (D)} = A'B'C + A'BC' + AB'C' + ABC = \Sigma(1,2,4,7)$$
$$\text{Borrow(Bout)} = A'B'C + A'BC' + A'BC + ABC = \Sigma(1,2,3,7)$$




 Q. Implement 4:16 decoder using 3:8 decoder.




Q. Implement 4:16 decoder using 2:4 decoder

A3	A2	A1	A0	HIGH OUTPUT
0	0	0	0	Y0
0	0	0	1	Y1
0	0	1	0	Y2
0	0	1	1	Y3
0	1	0	0	Y4
0	1	0	1	Y5
0	1	1	0	Y6
0	1	1	1	Y7
1	0	0	0	Y8
1	0	0	1	Y9
1	0	1	0	Y10
1	0	1	1	Y11
1	1	0	0	Y12
1	1	0	1	Y13
1	1	1	0	Y14
1	1	1	1	Y15

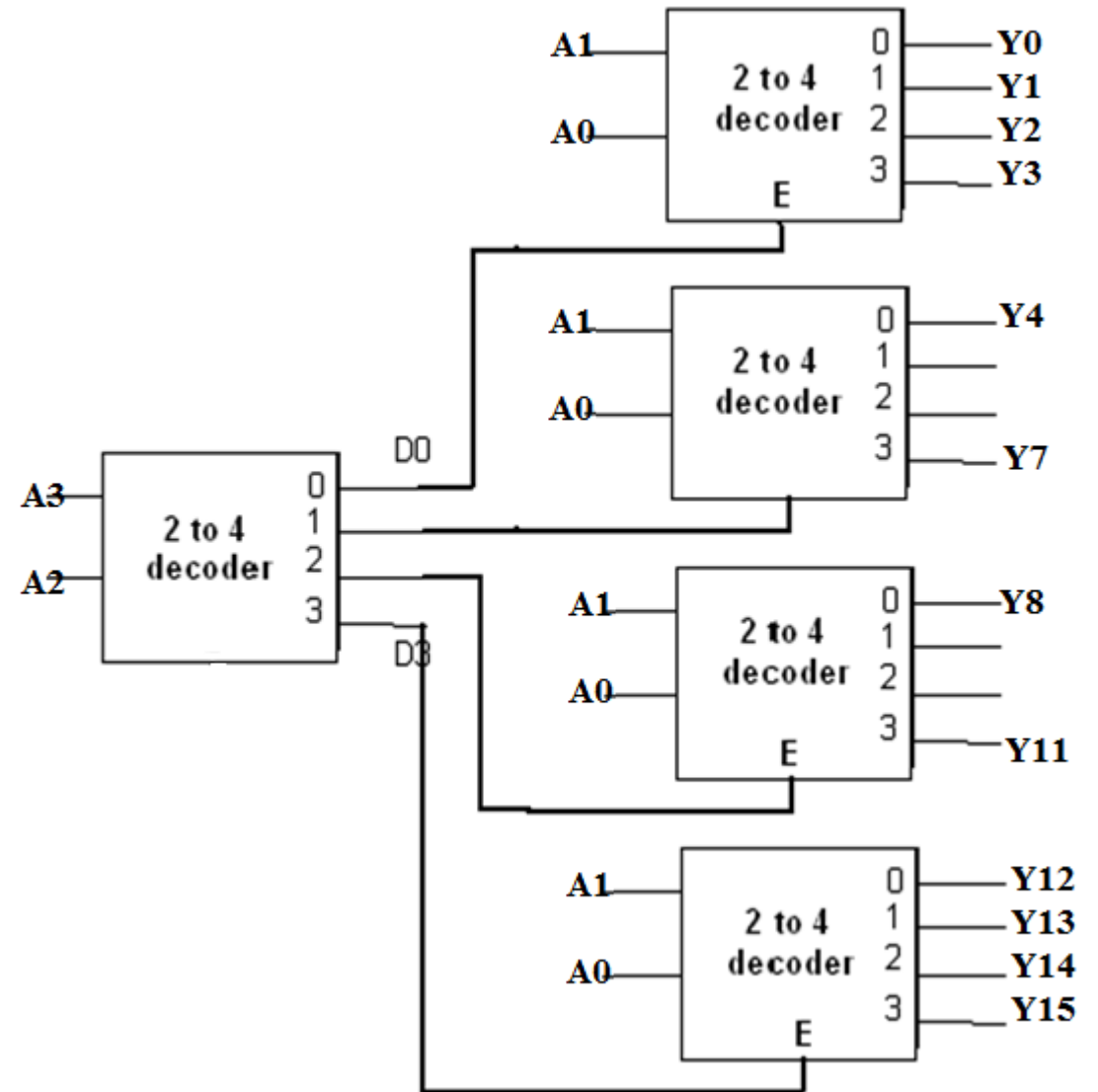


Encoder

 - Reverse operation of a Decoder.
- It has a maximum of 2^n input lines and 'n' output lines.
- It encodes the information from 2^n inputs into an n-bit code.
- It will produce a binary code equivalent to the input, which is active High.



Inputs				Outputs	
D_3	D_2	D_1	D_0	Q_1	Q_0
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1
0	0	0	0	x	x

 

MCQ

Which of the following is not valid encoder?

(A)

8 X 3

(B)

5 X 32

(C)

2 X 1

(D)

All are valid