

Unit-6

Sequential Logic Circuits : Applications

Register

Register

Flip-flop is a 1 bit memory cell which can be used for storing the **digital** data.



To increase the storage capacity in terms of number of bits, we have to use a group of flip-flop. Such a group of flip-flop is known as a **Register**.

The **n-bit register** will consist of **n** number of flip-flop and it is capable of storing an **n-bit** word.

Two Function of register

1. Data Storage

2. Date Movement

  

Shift Registers

- Another function of a register, besides storage, is to provide for *data movements*.
- Each *stage* (flip-flop) in a shift register represents one bit of storage,

And, shifting capability of a register permits the movement of data from stage to stage within the register, or into or out of the register upon application of clock pulses.








Application of shift register

- Shift register is used as **Parallel to serial converter**, which converts the parallel data into serial data. It is utilized at the **transmitter** section after Analog to Digital Converter ADC block.
- Shift register is used as **Serial to parallel converter**, which converts the serial data into parallel data. It is utilized at the **receiver** section before Digital to Analog Converter DAC block.
- Shift register along with some additional gates generate the sequence of zeros and ones. Hence, it is used as **sequence generator**.
- Shift registers are also used as **counters**.

There are two types of counters based on the type of output from right most D flip-flop is connected to the serial input. Those are **Ring counter** and **Johnson Ring counter**.

Shift Registers

       - Basic data movement in shift registers (four bits are used for illustration).



The Shift Register


The **Shift Register** used for the storage or the transfer of binary data.

Serial-in to Serial-out (**SISO**) - Data is shifted serially “IN” and “OUT” of the register, one bit at a time in either a left or right direction under clock control.


Serial-in to Parallel-out (**SIPO**) - Register is loaded with serial data, one bit at a time, with the stored data being available at the output in parallel form.


Parallel-in to Serial-out (**PISO**) - Parallel data is loaded into the register simultaneously and is shifted out of the register serially one bit at a time under clock control.

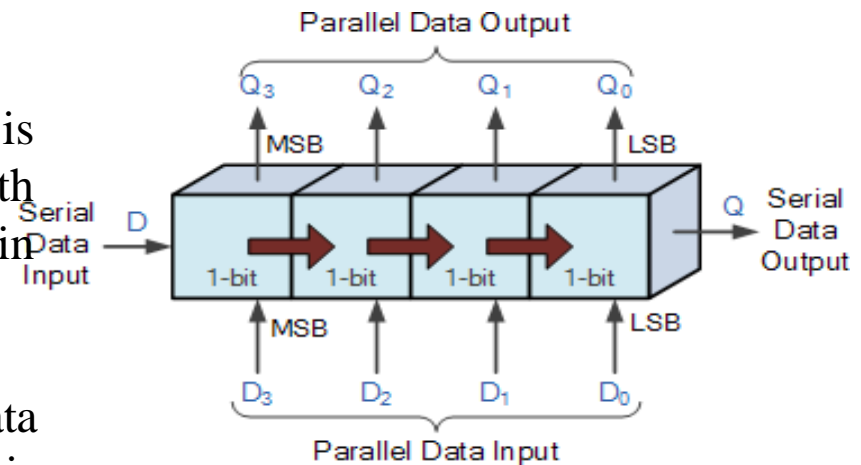Parallel-in to Parallel-out (**PIPO**) - Parallel data is loaded simultaneously into the register, and transferred together to their respective outputs by the same clock pulse.




SISO

 

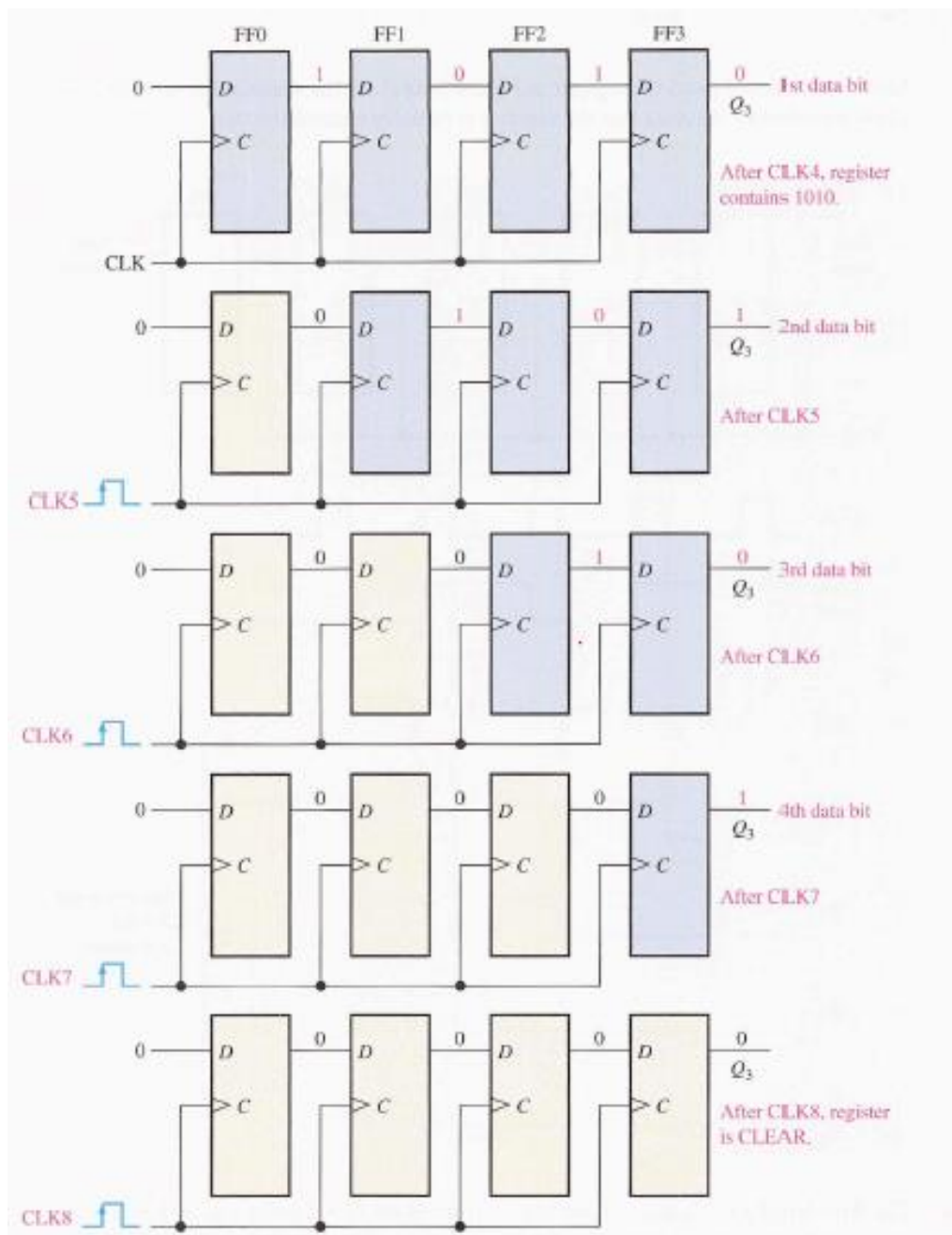

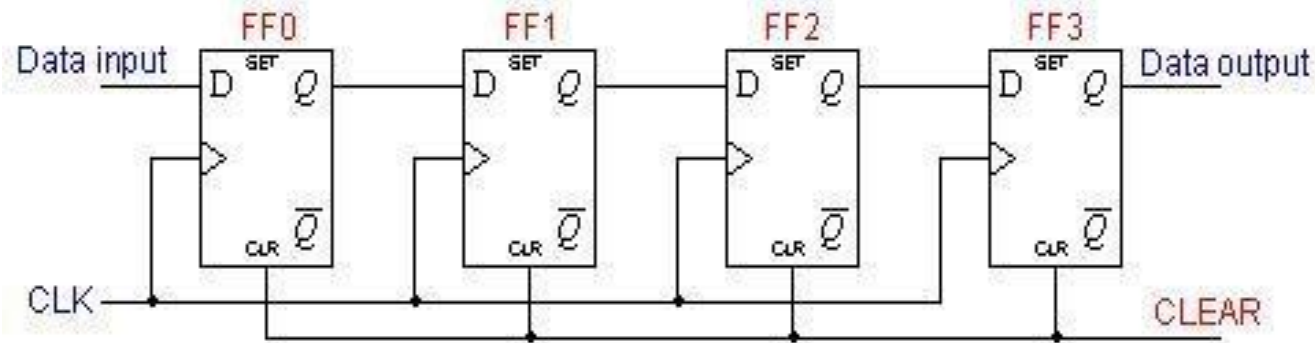Serial-in to Serial-out (SISO) Shift Register



All the FF are reset and a logical input 1011 is applied at the serial input line connected to stage FF0

Operation of the Shift-right Register					
Timing pulse	Q_A	Q_B	Q_C	Q_D	Serial output at Q_D
Initial value	0	0	0	0	0
After 1 st clock pulse	1	0	0	0	0
After 2 nd clock pulse	1	1	0	0	0
After 3 rd clock pulse	0	1	1	0	0
After 4 th clock pulse	1	0	1	1	1

MCQ

The group of bits 11001 is serially shifted (right-most bit first) into a 5-bit serial output shift register with an initial state 01110. After three clock pulses, the register contains _____ .


- a) 01110
- b) 00001
- c) 00101
- d) 00110

MCQ


Assume that a 4-bit serial in/serial out shift register is initially clear. We wish to store the nibble 1100. What will be the 4-bit pattern after the second clock pulse? (Right-most bit first)

 - a) 1100
- b) 0011
- c) 0000
- d) 1111

4-bit Serial-in to Parallel-out Shift Register



Clock Pulse No	QA	QB	QC	QD
0	0	0	0	0
1	1	0	0	0
2	0	1	0	0
3	0	0	1	0
4	0	0	0	1
5	0	0	0	0


 


MCQ


A serial in/parallel out, 4-bit shift register initially contains all 1s. The data nibble 0111 is waiting to enter. After four clock pulses, the register contains _____ .

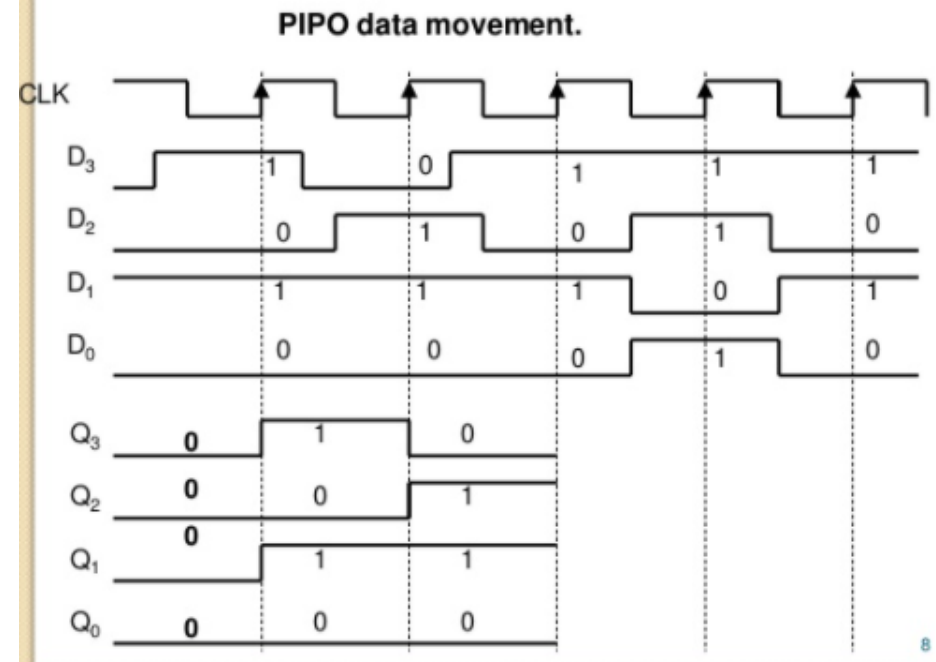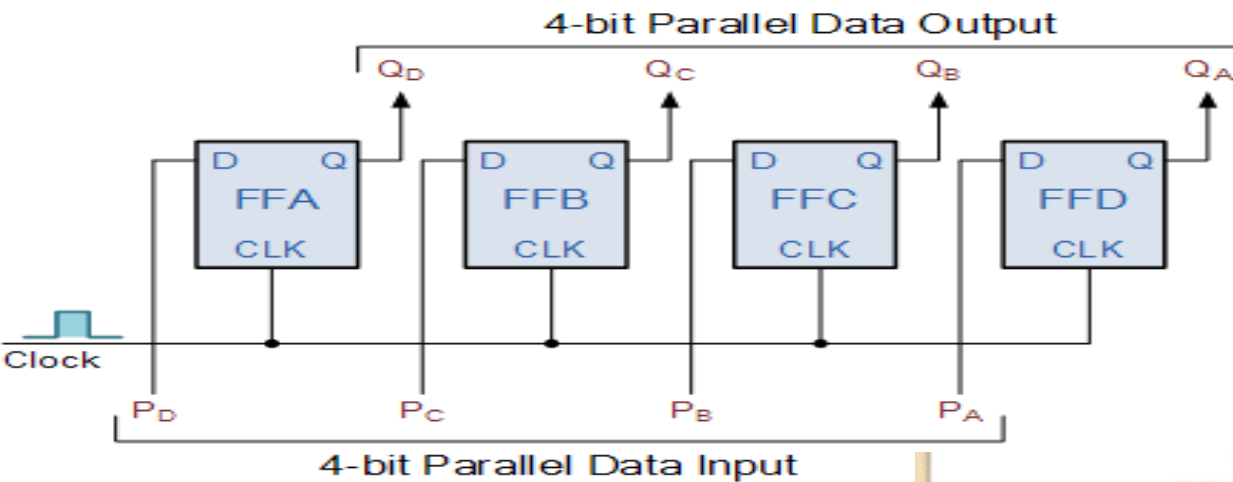- a) 0000
- b) 1111
- c) 0111
- d) 1000



4-bit Parallel-in to Parallel-out Shift Register



PISO Shift Register

 

(a) Logic diagram

  

Require 1 clk to load parallel data


Ring Counter

- It is a type of counter in which the output of the last flip flop is connected as an input to the first flip-flop is known as a *Ring counter*.
- The input is shifted between the flip-flops in a ring shape , so it is known as a Ring counter.
- A Ring counter is a **synchronous counter**.
The synchronous counter has a common clock signal that triggers all the Flip-flops at the same time.

Ring Counter

- Ring counter consists of D-flip flops connected in cascade setup with the output of last Flip-flop connected to the input of first Flip-flop.

 Ring counter has $\text{Mod} = n$ 'n' is the number of bits.
It means 4-bit ring counter has 4 states.



Clock Pulse	Q3	Q2	Q1	Q0
0	0	0	0	1
1	0	0	1	0
2	0	1	0	0
3	1	0	0	0

Ring counter divides the frequency of the clock signal by 'n'.

Merits

Can be implemented using D and JK flip-flops. It is a self-decoding circuit.

Demerits

A ring counter of n-bits has only n valid states instead of 2^n .


This makes them inefficient in terms of state-usage.

MCQ

- . the number of flip flops required for a mod 16 ring counter are
 - A. 4 flip flops
 - B. 8 flip flops
 - C. 10 flip flops
 - D. 16 flip flops

Johnson or Twisting Ring Counter

 - The Johnson counter is a modification of ring counter.
- In this the inverted output of the last stage flip flop is connected to the input of first flip flop.
- If we use **N** flip flops to design the Johnson counter, it is known as **2N** bit Johnson counter or **Mod 2N** Johnson counter.



Q _A	Q _B	Q _C	Q _D
0	0	0	0
1	0	0	0
1	1	0	0
1	1	1	0
1	1	1	1
0	1	1	1
0	0	1	1
0	0	0	1
repeat			

Last FF output($\sim Q$) feed back input to first FF

Count 2n clock pulse

MOD-2N counter

This is an advantage of the Johnson counter that it requires only half number of flip flops that of a ring counter uses, to design the same Mod.

Johnson counter divides a clock signal's frequency by ' $2N$ '.

N is the bit size of the counter.

MCQ

Ring shift and Johnson counters are _____ .

- a) Synchronous counters
- b) Asynchronous counters
- c) True binary counters
- d) Synchronous and true binary counters

MCQ

In a 4-bit Johnson counter sequence, there are a total of how many states or bit patterns?

- a) 1
- b) 3
- c) 4
- d) 8